

# Lab 5: OpAmps II

## Objective:

- Photodiodes
- Transimpedance Amplifier (TIA)
- Transconductive Amplifier (TCA)

## Lab Exercises:

### **A. Photodiode Basics (30min estimated amount of time)**

- [L1] At three different light levels create an IV curve for the photodiode. Plot all 3 IV curves on the same plot.
- [L2] What differences do you notice about the 3 different IV curves relative to the light levels?

### **B. Current to Voltage Converter (Transimpedance Amplifier) (45min estimated amount of time)**

Build the circuit in Figure 1. Use an LF356 op-amp, and arrange the dual-output power supply to supply +15 V<sub>DC</sub> to pin 7, -15 V<sub>DC</sub> to pin 4, and ground to pin 3.

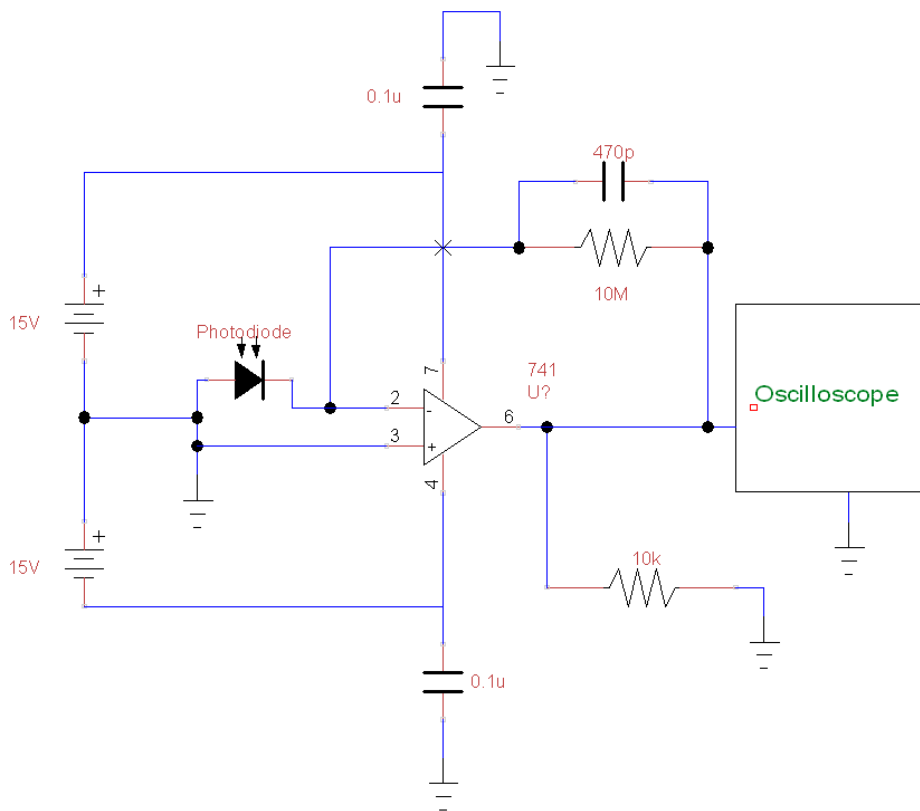


Figure 1. Transimpedance Amplifier (TIA) Circuit

If you see an oscillation in your measurement please perform the section in italics.

*Look at the output of the TIA on the oscilloscope. What do you see? The circuit might be oscillating at a very high frequency, which is not a good thing!*

**[L3]**      *Measure the frequency of oscillation, in MHz.*

*To get rid of this oscillation, place 0.1 $\mu$ F capacitors from the supply pins to ground (from pin 7 to ground, and from pin 4 to ground). These capacitors are small yellow disks marked "104M". They are non-polarized—it doesn't matter which way they are installed. Look at the output on the oscilloscope. Has the high frequency oscillation disappeared?*

Cover the photodiode with a black cloth to block all of the light.

**[L4]**      What do you observe on the oscilloscope?

**[L5]**      What DC voltage  $V_o$  do you measure?

Expose the photodiode to light from the overhead fluorescent lights. Replace the feedback resistor with other values to make sure that the output voltage is less than  $\pm 15$ VDC.

**[L6]**      What do you observe on the oscilloscope?

**[L7]**      What is the frequency of oscillation?

**[L8]**      What DC voltage  $V_o$  do you measure?

**[L9]**      What is the value of the feedback resistor that you used?

**[L10]**     What is the photocurrent,  $I_{ph}$  in  $\mu$ A?

Expose the photodiode to light from the portable fluorescent light.

**[L11]**     What do you observe on the oscilloscope?

**[L12]**     What is the frequency of oscillation?

**[L13]**     What DC voltage  $V_o$  do you measure?

### **C. Simple Transconductance (Voltage to Current) Amplifier (45 estimated amount of time)**

Use a 0-5V triangle wave as  $V_{in}$ . Set the frequency low ( $\sim 10$ Hz) so you can visibly see the LED flashing for troubleshooting.

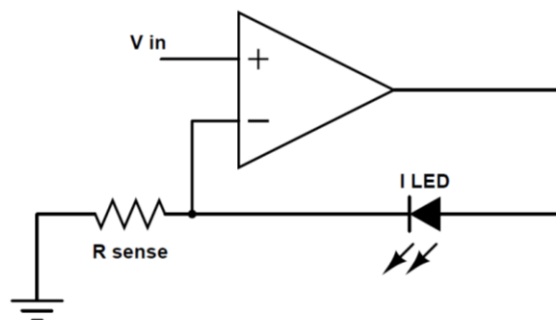


Figure 2. Transconductance Amplifier (TCA) Circuit

- Wire up the TCA circuit (Figure 3) using a 5mm LED (any color).
  - Choose  $R_{\text{sense}}$  so that  $(I_{\text{LED}} / V_{\text{in}}) \leq 5\text{mA/V}$ .
    - The  $I_{\text{out}} / V_{\text{in}}$  is known as *transconductance*
  - Use  $V_{\text{CC}} = 10\text{V}$  for the OpAmp
- Measure the voltage drop across  $R_{\text{sense}}$  using Oscilloscope Channel 2.
  - The result should equal  $V_{\text{in}}$
- Now replace the single LED with three LEDs in series.

**[L14]** Sketch  $I_{\text{out}}$  vs  $V_{\text{in}}$  when there are 3 LEDs in the circuit. Comment on the result.

Go back to driving only a single LED

**[L15]** Does the current change compared to driving only 1 LED? Why or why not?