

Solutions

Opti 501

Problem 26)

$$a) I(t) = C_1 \frac{dV_1(t)}{dt} \quad t > 0^+$$

$$V_0 = RI(t) + V_1(t) = RC_1 \frac{dV_1(t)}{dt} + V_1(t) \Rightarrow V_1(t) = V_0 + [V_1(t=0^+) - V_0] e^{-t/RC_1}$$

Note that the coefficients in the above expression for $V_1(t)$ are chosen such that at $t=0^+$ the capacitor's voltage is $V_1(t=0^+)$, while at $t=\infty$ the capacitor's voltage is V_0 , that is, the battery's voltage.

$$I(t) = C_1 \frac{dV_1(t)}{dt} = \frac{1}{R} [V_0 - V_1(t=0^+)] e^{-t/RC_1} = \frac{1}{R} (V_0 - \frac{C_0}{C_1} V_0) e^{-t/RC_1} \Rightarrow$$

$$I(t) = \frac{C_1 - C_0}{RC_1} V_0 e^{-t/RC_1}$$

$$b) \text{ Energy delivered to the circuit by battery} = \int_{t=0}^{\infty} V_0 I(t) dt =$$

$$\frac{C_1 - C_0}{RC_1} V_0^2 \int_0^{\infty} e^{-t/RC_1} dt = (C_1 - C_0) V_0^2$$

$$c) \text{ Energy consumed in resistor} = \int_0^{\infty} RI^2(t) dt = \frac{(C_1 - C_0)^2}{RC_1^2} V_0^2 \int_0^{\infty} e^{-2t/RC_1} dt$$

$$= \frac{(C_1 - C_0)^2}{2C_1} V_0^2$$

d) At $t=0$, the \vec{E} -field acting on each plate of the capacitor is $\frac{1}{2}E_0$, and the charge on each plate is Q_0 ; therefore, the effective force on each plate is $\frac{1}{2}Q_0E_0$, trying to pull the plates together. This force does mechanical work on the outside world when the distance between plates is reduced from d_0 to d_1 . The amount of this mechanical work is given by:

$$\begin{aligned} \text{Mechanical work on the outside world} &= \frac{1}{2} Q_0 E_0 (d_0 - d_1) \\ &= \frac{1}{2} (C_0 V_0) (V_0 / d_0) (d_0 - d_1) = \frac{1}{2} C_0 V_0^2 (1 - \frac{d_1}{d_0}) = \frac{1}{2} C_0 V_0^2 (1 - \frac{C_0}{C_1}) \\ &= \frac{1}{2} (\frac{C_0}{C_1}) (C_1 - C_0) V_0^2 \end{aligned}$$

e) Energy delivered to capacitor by battery = energy delivered to the entire circuit - Energy consumed by the resistor =

$$(C_1 - C_0)V_0^2 - \frac{(C_1 - C_0)^2}{2C_1}V_0^2 = \frac{1}{2} \left(1 + \frac{C_0}{C_1}\right) (C_1 - C_0)V_0^2$$

(The same result may be obtained by computing $\int_0^{\infty} V_c(t) I(t) dt$ directly.)

(Energy delivered to capacitor by battery) - (Mechanical work done by capacitor on the outside world) = $\frac{1}{2} \left(1 + \frac{C_0}{C_1}\right) (C_1 - C_0)V_0^2 - \frac{1}{2} \left(\frac{C_0}{C_1}\right) (C_1 - C_0)V_0^2 = \frac{1}{2} (C_1 - C_0)V_0^2$.

This is equal to the change in the stored energy within the capacitor, namely, $W_1 - W_0 = \frac{1}{2} C_1 V_0^2 - \frac{1}{2} C_0 V_0^2 = \frac{1}{2} (C_1 - C_0)V_0^2$. ✓