

Problem 4) a) The current flowing through the circuit is related to the voltage across the capacitor via $i(t) = C\dot{v}_c(t)$. According to Kirchhoff's voltage law, the sum of the resistor voltage $Ri(t)$ and the capacitor voltage $v_c(t)$ must equal the applied voltage $v(t)$. Therefore,

$$RC\dot{v}_c(t) + v_c(t) = v(t) \quad \rightarrow \quad \tau(t)\dot{v}_c(t) + v_c(t) = v(t). \quad (1)$$


b) The above differential equation is similar to the 1st order ODE that has been analyzed in Sec.2. Using Eq.(3), Sec.2, we find

$$\begin{aligned} g(t) &= [1/\tau(t)] \exp[\int dt/\tau(t)] = \frac{1}{\tau_0[1 + \alpha \cos(\omega t)]} \exp\left(\frac{1}{\tau_0} \int_{-\infty}^t \frac{dt'}{1 + \alpha \cos(\omega t')}\right) \\ &= \frac{1}{\tau_0[1 + \alpha \cos(\omega t)]} \exp\left(\frac{1}{\tau_0 \omega} \int_{-\infty}^{\omega t} \frac{d\theta}{1 + \alpha \cos \theta}\right). \end{aligned} \quad (2)$$

The integral appearing in the exponent on the right-hand side of Eq.(2) was evaluated in Chapter 3, Section 2, Example 6. We thus have

$$g(t) = \frac{1}{\tau_0[1 + \alpha \cos(\omega t)]} \exp\left(\frac{2 \tan^{-1}[\sqrt{(1-\alpha)/(1+\alpha)} \tan(\omega t/2)]}{\sqrt{1-\alpha^2} \tau_0 \omega}\right). \quad (3)$$

When $\alpha = 0$, Eq.(3) reduces to $g(t) = (1/\tau_0) \exp(t/\tau_0)$, in agreement with the results obtained in Example 3, Sec.2. When $0 < |\alpha| < 1$, the coefficient of $\tan(\omega t/2)$ will be some positive number other than 1. Here one must be careful, because the arctangent function has $\pm\pi$ discontinuities whenever ωt passes through an odd-multiple of π . Nevertheless, once the angles have been unwrapped, the exponent of $g(t)$ becomes a periodically wobbling function of t , such as that shown on the right. The exponent rises continually with time as $t/(\sqrt{1-\alpha^2}\tau_0)$, albeit with a superposed periodic wobble whose frequency is ω and whose amplitude depends on α , being greater for larger values of $|\alpha|$. The subsequent division of the exponential function by $\tau_0[1 + \alpha \cos(\omega t)]$, as required by Eq.(3), further modulates the exponential function by multiplying it with a periodic function of time whose frequency also happens to be ω .

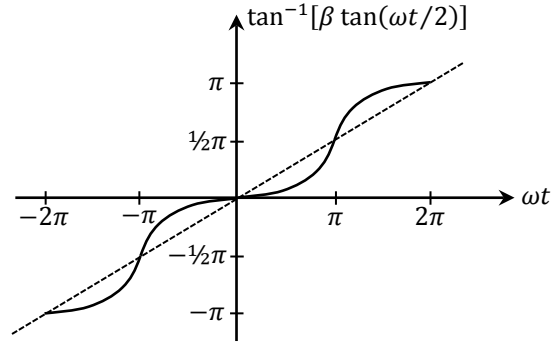

Substitution of the function $g(t)$ given by Eq.(3) above into Eq.(4), Sec.2, finally yields

$$v_c(t) = \int_{-\infty}^t \exp\left(-\frac{2 \tan^{-1}[\sqrt{(1-\alpha)/(1+\alpha)} \tan(\omega t/2)]}{\sqrt{1-\alpha^2} \tau_0 \omega}\right) g(t')v(t')dt'. \quad (4)$$

Aside from wiggles of frequency ω that the integrand in the above equation has inherited from the oscillations of the circuit parameters, the final result in Eq.(4) is qualitatively similar to that for an RC circuit having a time-invariant $\tau = RC$, as given by Eq.(9) in Example 3, Sec.2.